

Datapath Design

Book of John P. Hayes

Pg 240-244


Book of David A. Patterson

Pg 183-189


Combinational Array Multiplier

- ✓ Composed of arrays of simple combinational elements, each of which implements an add/sub and shift operation for small slices of the multiplicand operands.
- ✓ $X = x_{n-1}x_{n-2}\dots x_1x_0$ and $Y = y_{n-1}y_{n-2}\dots y_1y_0$ where both X and Y are unsigned integers. Now $P = X \times Y$ can be expressed as $P = \sum_{i=0}^{n-1} 2^i x_i Y$ which can be rewritten as $P = \sum_{i=0}^{n-1} 2^i \left(\sum_{j=0}^{n-1} x_i y_j 2^j \right)$
- ✓ It requires $n \times n$ array of 2-input AND gate.
- ✓ The product terms are summed by an array of $n(n-1)$ 1-bit full adders.

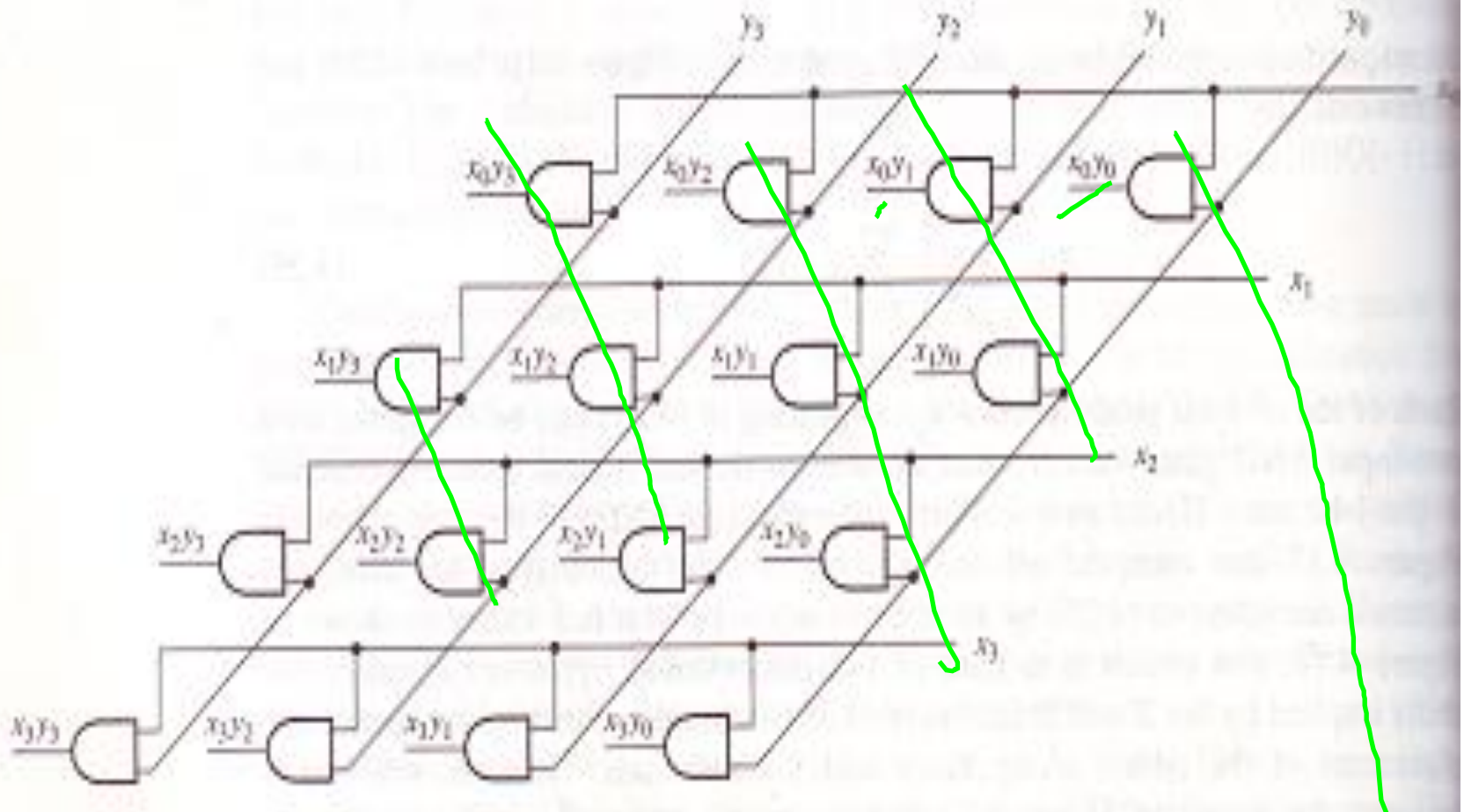AND Array for 4×4 bit Unsigned Multiplication




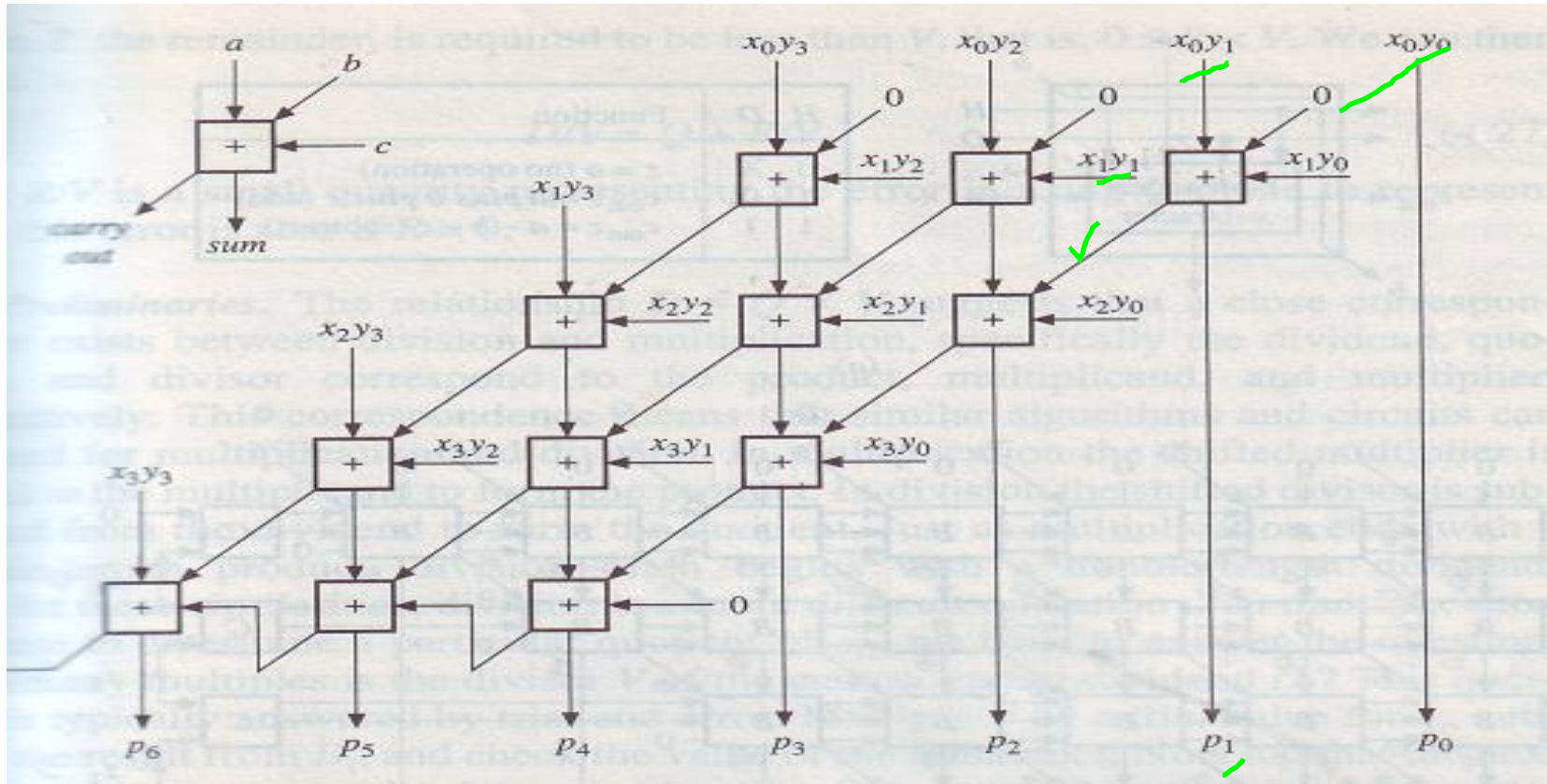Full Adder Array for 4×4 bit Unsigned Multiplication



Array Implementation for Booth Multiplication

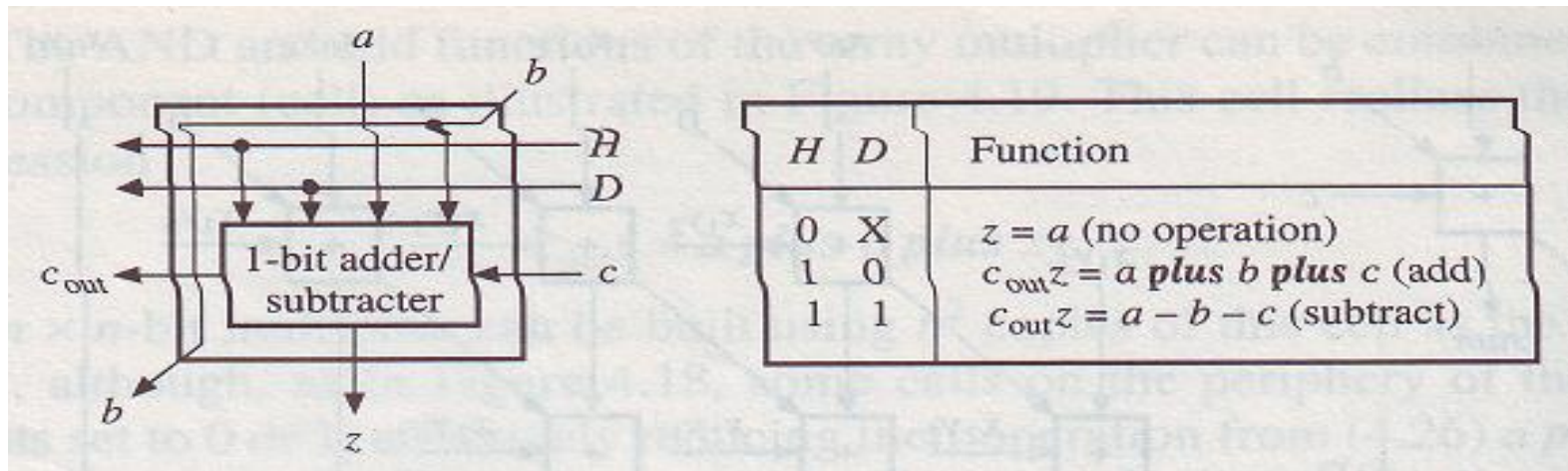- ✓ It requires a multifunction cell capable of addition, subtraction and no operation (skip).



- ✓ The functions of B are defined by $z = a \text{ xor } bH \text{ xor } cH$ and $C_{out} = (a \text{ xor } D)(b+c) + bc$
- ✓ An n-bit multiplier is constructed from $n^2 + n(n-1)/2$ copies of the B Cell.

Array Implementation for Booth Multiplication

- ✓ When $HD = 10$ the equations reduce to full adder equations.
$$z = a \text{ xor } b \text{ xor } c \text{ and } c_{\text{out}} = ab + ac + bc$$
- ✓ When $HD = 11$ the equations reduce to full subtracter equations:
$$z = a \text{ xor } b \text{ xor } c \text{ and } c_{\text{out}} = \bar{a}b + \bar{a}c + bc$$
- ✓ When $H = 0$ then $z = a$ and carry plays no role in the final result.
- ✓ A $n \times n$ bit multiplier is constructed from $n^2 + n(n-1)/2$ cells.


Array Implementation for Booth Multiplication

- ✓ C cell generates control input H and D required by the B cells depending on the combination of $x_i x_{i-1}$.

$$H = x_i \oplus x_{i-1}$$
$$D = x_i \bar{x}_{i-1}$$

x_i	x_{i-1}	H	D
0	0	0	0
0	1	1	0
1	0	1	1
1	1	0	0

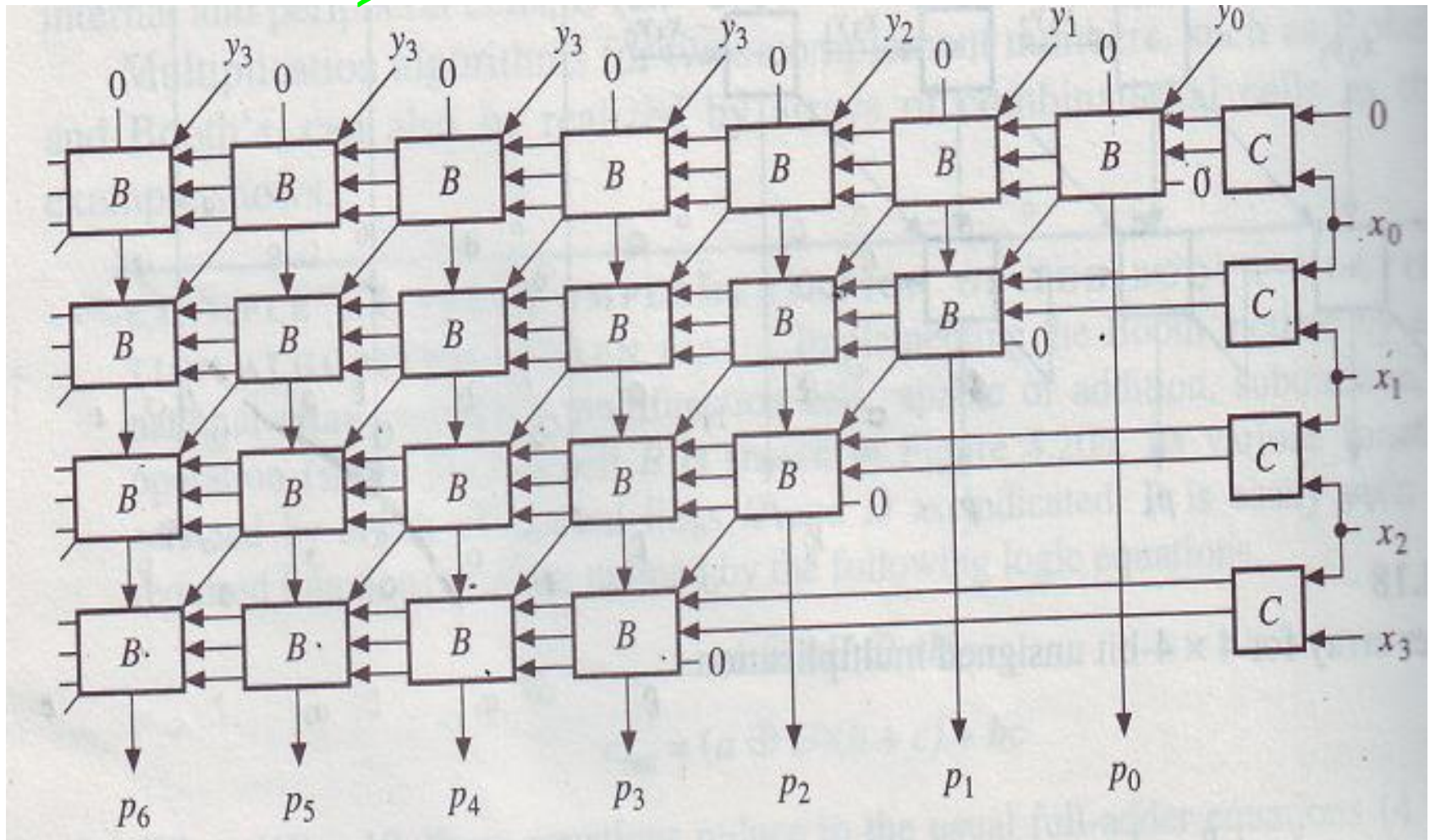Combinational Array implementing the Booth's Algorithm




Division

A handwritten long division problem on a light blue grid background. The divisor is 1000_{ten} and the dividend is 1001010_{ten}. The quotient is 1001_{ten}. The remainder is 10_{ten}. The steps shown are: 1000 goes into 1001 one time, subtract 1000 from 1001 to get 10. Bring down the next digit 0 to get 101. 1000 goes into 1010 one time, subtract 1000 from 1010 to get 10. Bring down the next digit 1 to get 101. 1000 goes into 1010 one time, subtract 1000 from 1010 to get 10. The final remainder is 10.

	1001 _{ten}	Quotient
Divisor 1000 _{ten}	$\overline{)1001010_{ten}}$	Dividend
	$\underline{-1000}$	
	10	
	101	
	1010	
	$\underline{-1000}$	
	10 _{ten}	Remainder


✓ Dividend = Quotient \times Divisor + Remainder

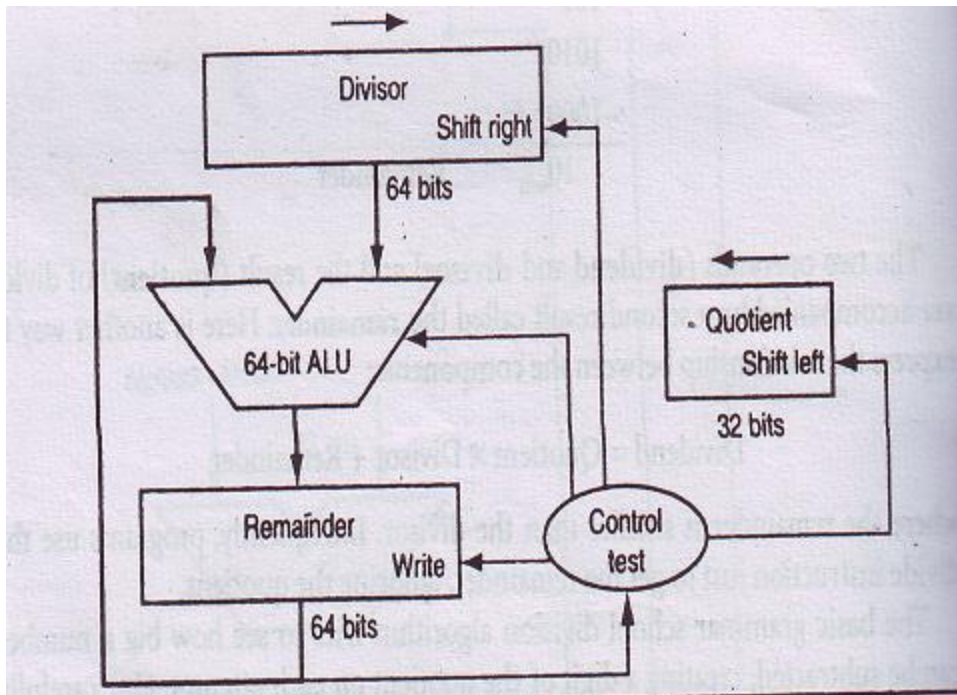Division Algorithm and Hardware for Unsigned Number



Read the improved version of the circuit by yourself.

$[n+1]$ it

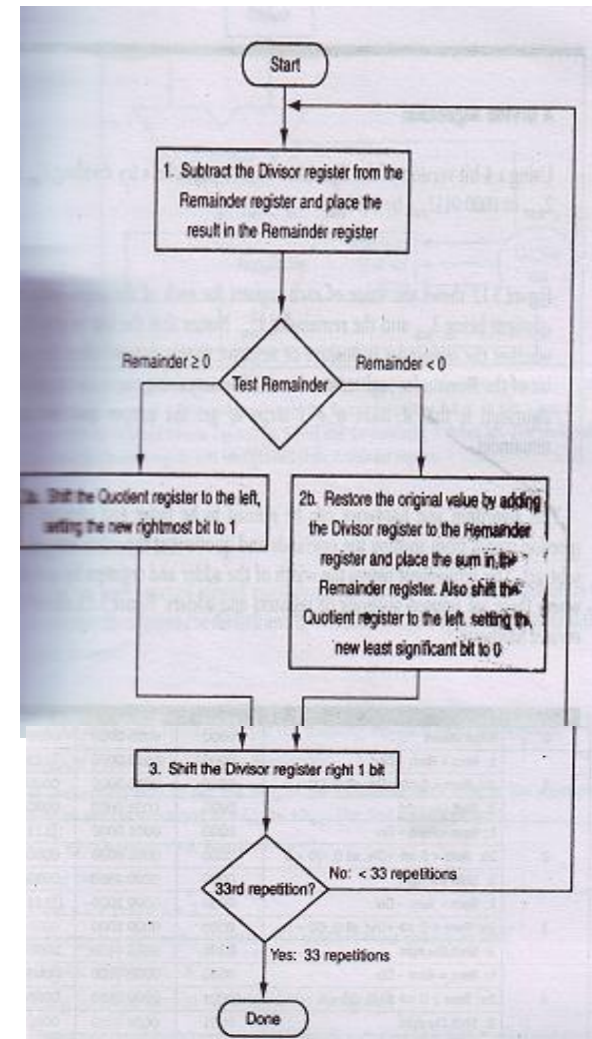

2) 7/3
6/1

Example

2 7

Iteration	Step	Quotient	Divisor	Remainder
0	Initial values	0000	0010 0000	0000 0111
1	1: Rem = Rem - Div	0000	<u>0010</u> 0000	①110 0111
	2b: Rem < 0 \Rightarrow +Div, sll Q, Q0 = 0	0000	0010 0000	0000 0111
	3: Shift Div right	0000	0001 0000	0000 0111
2	1: Rem = Rem - Div	0000	0001 0000	①111 0111
	2b: Rem < 0 \Rightarrow +Div, sll Q, Q0 = 0	0000	0001 0000	0000 0111
	3: Shift Div right	0000	0000 1000	0000 0111
3	1: Rem = Rem - Div	0000	0000 1000	①111 1111
	2b: Rem < 0 \Rightarrow +Div, sll Q, Q0 = 0	0000	0000 1000	0000 0111
	3: Shift Div right	0000	0000 0100	0000 0111
4	1: Rem = Rem - Div	0000	0000 0100	①000 0011
	2a: Rem \geq 0 \Rightarrow sll Q, Q0 = 1	0001	0000 0100	0000 0011
	3: Shift Div right	0001	0000 0010	0000 0011
5	1: Rem = Rem - Div	0001	0000 0010	①000 0001
	2a: Rem \geq 0 \Rightarrow sll Q, Q0 = 1	0011	0000 0010	0000 0001
	3: Shift Div right	<u>0011</u>	0000 0001	0000 0001

3

1