

Pipeline Processing

Book of John P. Hayes

pp: 275 - 283


Pipeline Processing

- ✓ It is a general technique for increasing processor throughput without requiring large amount of extra hardware.
- ✓ Used in the design of the complex datapath units such as multiplier and floating-point adders.

Pipeline Processor

- ✓ It consists of a sequence of m -data processing circuits, called stages or segments, which collectively perform a single operation on a stream of data operands passing through them.
- ✓ Some processing is performed at each stage, but a final result is obtained only after an operand set has passed through the entire pipeline.
- ✓ In each clock cycle, every stage transfer its previous results to the next stage and computes a new set of results.

Structure of a Pipeline Processor

 

Pipeline Processor

- ✓ An m -stage pipeline can simultaneously process up to m independent sets of data operands.
- ✓ Suppose that each stage of the m -stage pipeline takes T seconds to perform its local sub-operation and store its results. Then T is pipeline's clock period.
- ✓ The *delay or latency* of the pipeline, is the time to complete a single operation, that is mT .
- ✓ Any operation that can be decomposed into a sequence of sub-operations of about the same complexity can be realized by a pipeline processor.

Example

✓ The addition of two normalized floating-point numbers x and y can be implemented by four step sequence:

1. compare the exponents.
2. Align the mantissa.
3. Add the mantissa.
4. Normalize the result.


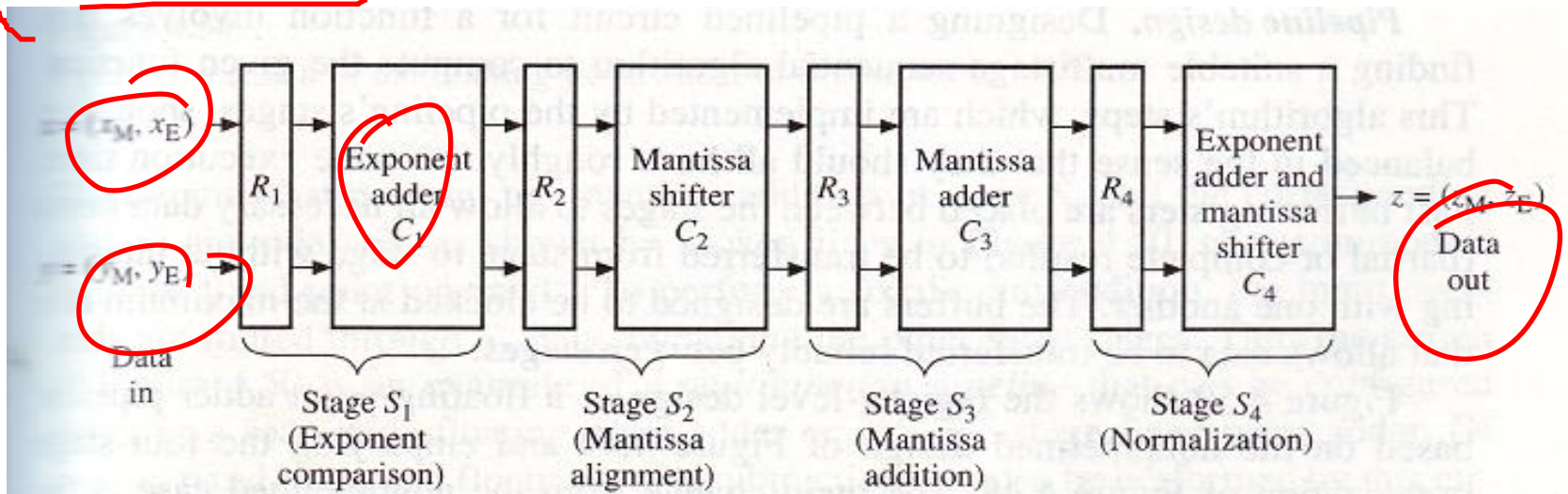


Figure: Four stage floating-point adder pipeline

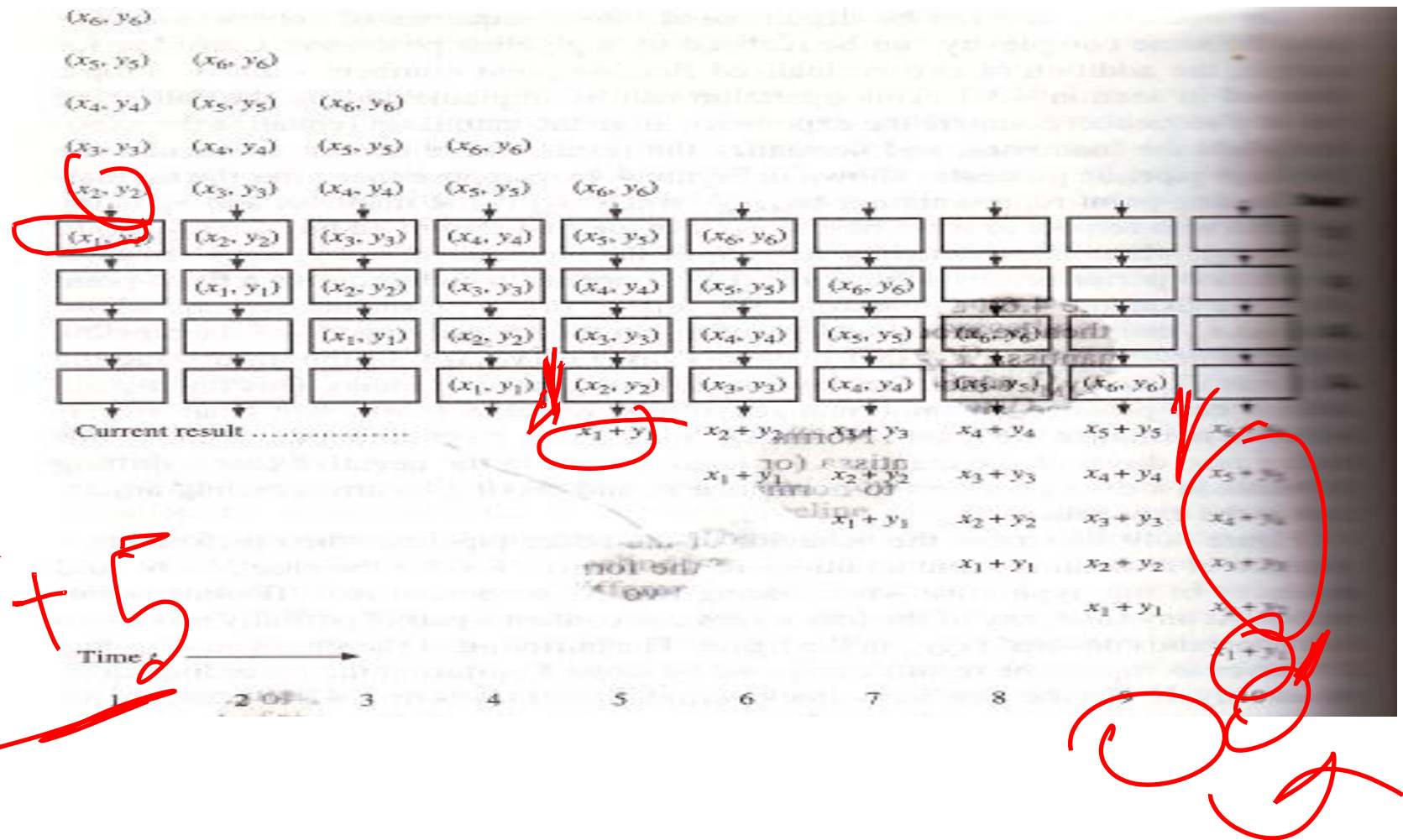Operation of the Four Stage Floating-point Adder Pipeline



Performance Analysis of Four Stage Floating-point Adder Pipeline

- ✓ If T is the pipeline's clock period, then the pipeline's delay is $4T$.
- ✓ $4T$ = time required to do one floating-point addition using a non-pipelined processor plus the delay due to the buffer registers.
- ✓ N consecutive additions can be done in time $(N+3)T$ using the pipelined processor.
- ✓ Speed up $S(4) = 4N / (N+3)$
- ✓ For large N , $S(4) \approx 4$.


$$4 + \frac{4 \times (N-1)}{N+3} = 6 + \frac{2}{N+3}$$

Pipeline Design

- ✓ Designing a pipelined circuit for a function involves first finding a suitable multistage sequential algorithm to compute the given function.
- ✓ This algorithm steps should be balanced.
- ✓ Fast buffers are placed between the stages.
- ✓ The buffers are designed to be clocked.




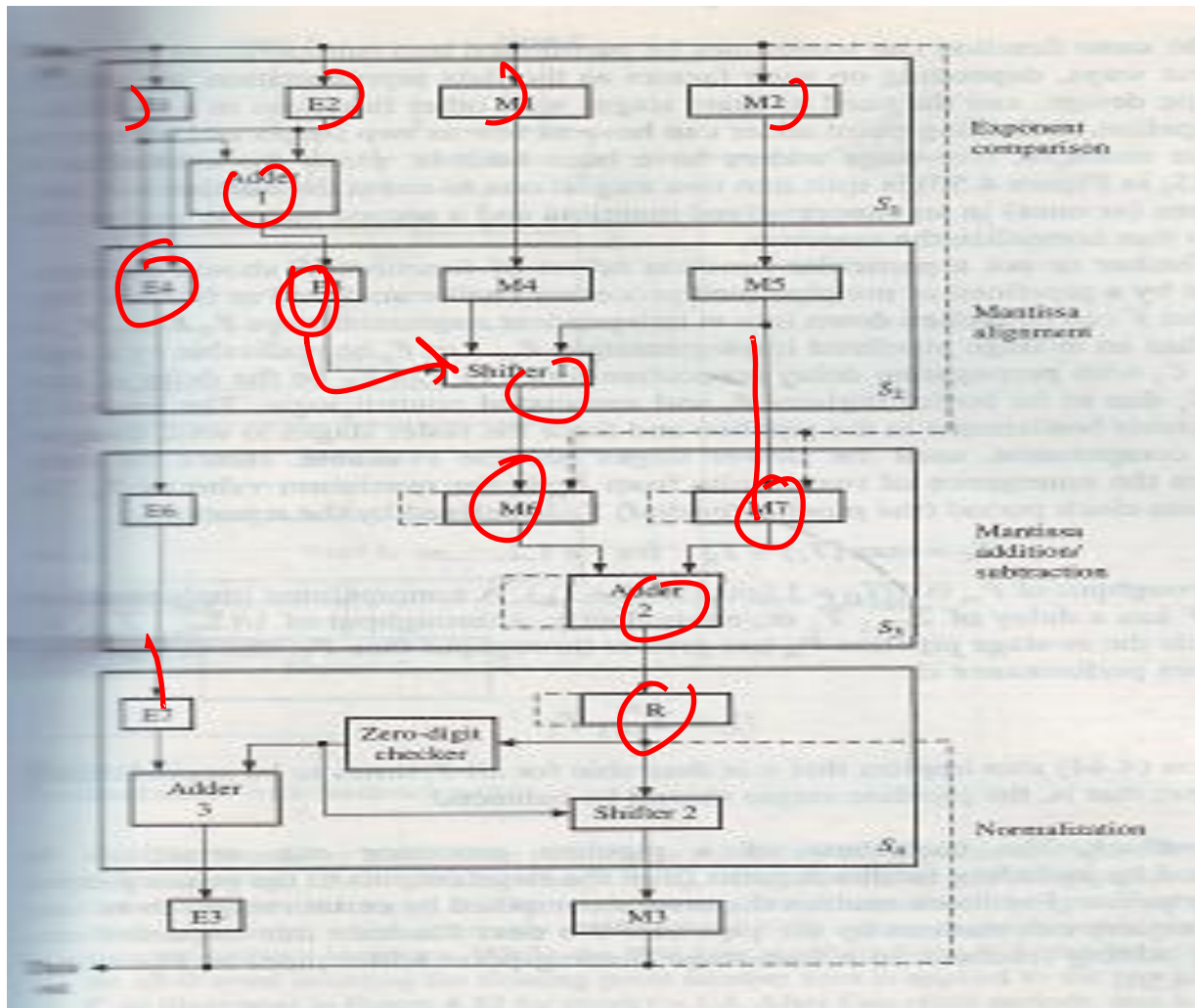Pipelined Version of the Floating-point/ Fixed-point Adder




Feedback

 - ✓ The usefulness of a pipeline processor can be enhanced by including feedback paths from the stage outputs to the primary inputs of the pipeline.
- ✓ It enables the results computed by certain stages to be used in subsequent calculations.




Summation by a Pipeline Processor

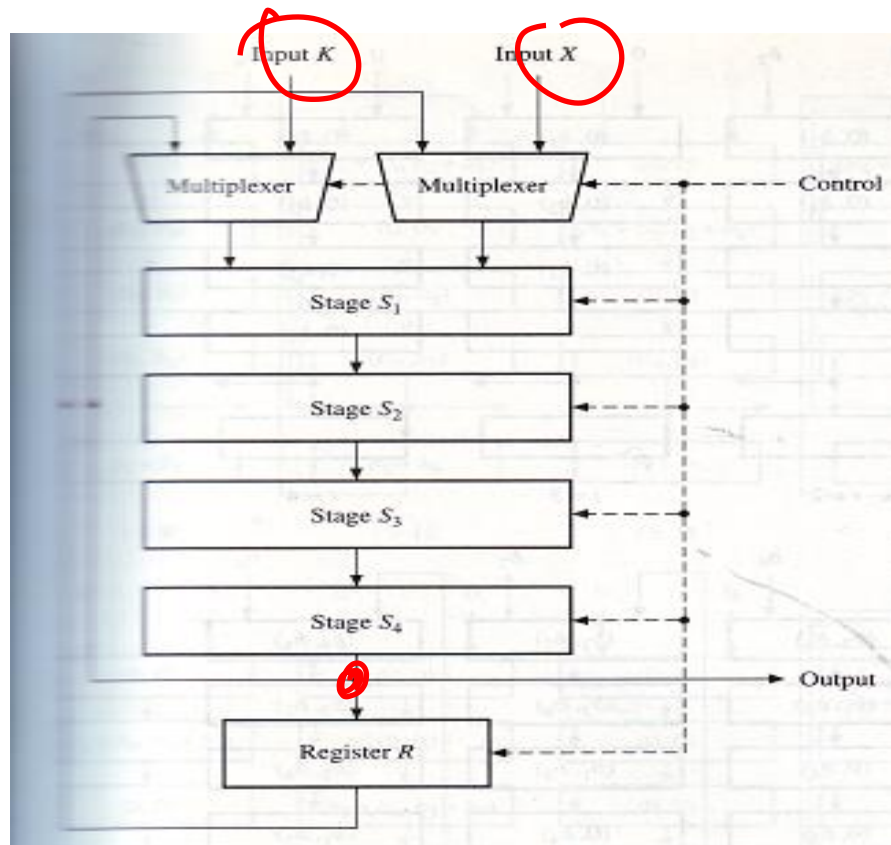
- ✓ Problem: compute the summation of 8 floating-point number $b_1, b_2, b_3, b_4, b_5, b_6, b_7$ and b_8 .




Summation by a Pipeline Processor

 

Summation by a Pipeline Processor

 

Summation by a Pipeline Processor

 

Summation by a Pipeline Processor

