

Lecture 2


Datapath Design

Book of John P. Hayes

Fixed-Point Arithmetic

- ✓ Addition
- ✓ Subtraction
- ✓ Multiplication
- ✓ Division

Half Adder

 


(a) Half Adder

$X_0 Y_0$	$S_0 C_0$
0 0	0 0
0 1	1 0
1 0	1 0
1 1	0 1

(b) Truth Table

$$S_0 = X_0 \text{ xor } Y_0 \text{ and } C_0 = X_0 Y_0$$

Full Adder

 

(a) Full Adder

Inputs			Outputs	
x_0	y_0	c_{-1}	c_0	s_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


(b) Truth Table

$$s_0 = x_0 \text{ xor } y_0 \text{ xor } c_{-1}$$


$$c_0 = x_0 y_0 + x_0 c_{-1} + y_0 c_{-1}$$

$$x_0 y_0 + c_0 (x_0 \oplus y_0)$$

Full Adder

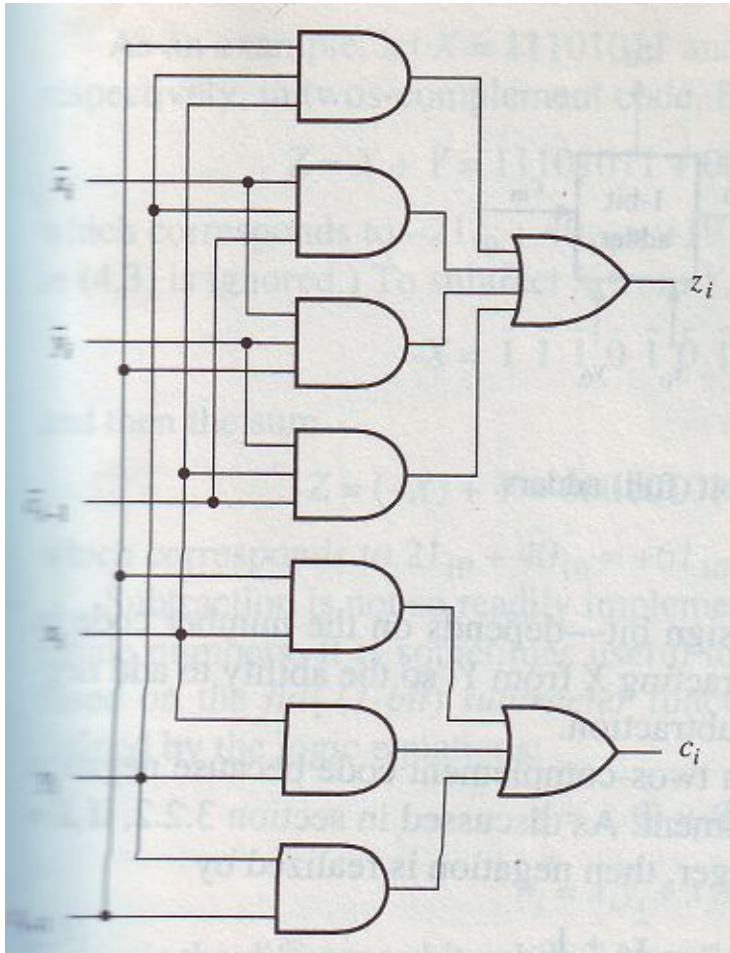


(a) Two-level AND-OR logic circuit

 


(b) Symbol

Serial Binary Adder

 

- ✓ Least expensive circuit in terms of hardware cost.
- ✓ It adds the numbers bit by bit and so requires n clock cycle to compute the sum of two n-bit numbers.
- ✓ Circuit size is independent of n.


Ripple Carry Adder / Parallel Adder

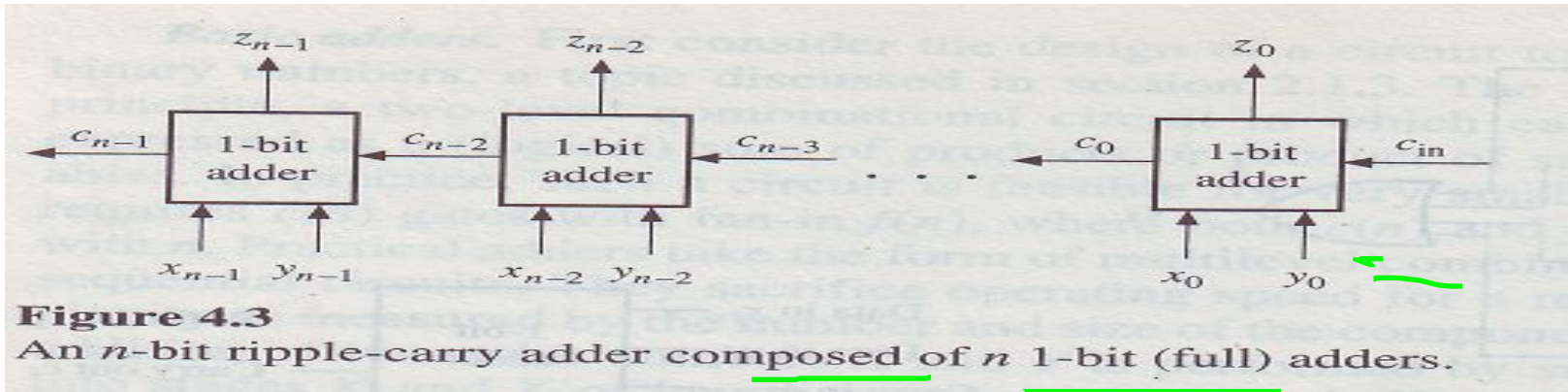

- ✓ A 1 appearing on the carry in line of a 1-bit adder cause it to generate a 1 on its carry out line. So, the carry signal propagate through the adder from right to left.
- ✓ The maximum signal propagation delay is nd , where d is the delay of a full-adder stage.
- ✓ The amount of hardware increase linearly with n .


Subtractor for 2's Complement Number

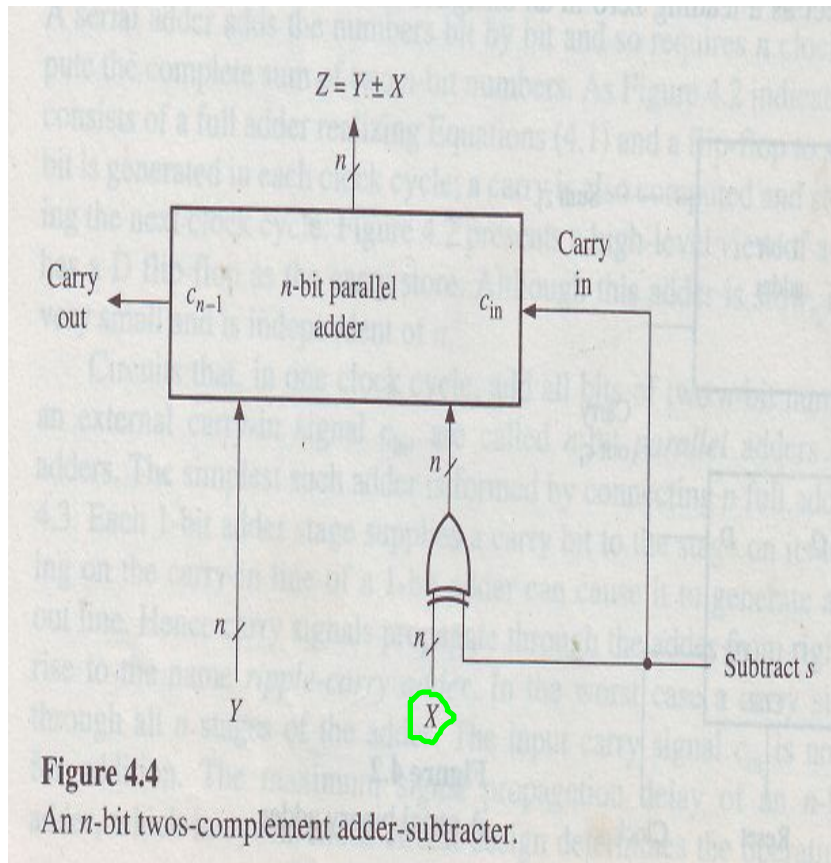- ✓ When $s = 0$ then $X \text{ xor } s = X$
- ✓ When $s = 1$ then $X \text{ xor } s = \overline{X}$




Subtractor for 2's Complement Number

Example: Adder/Subtractor

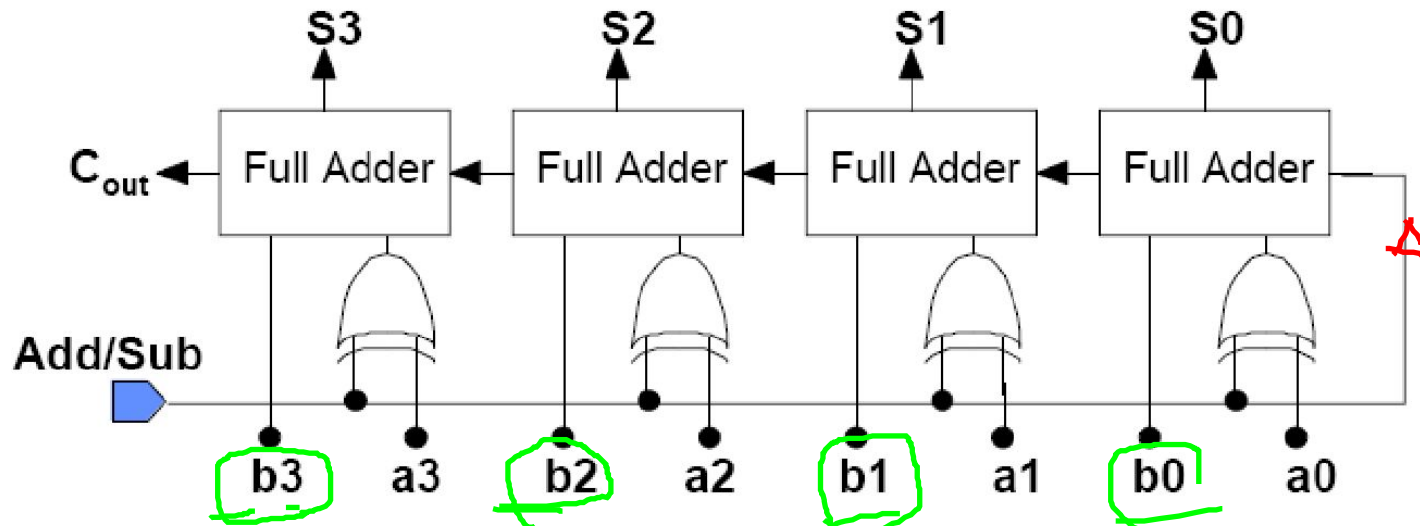

Subtractor

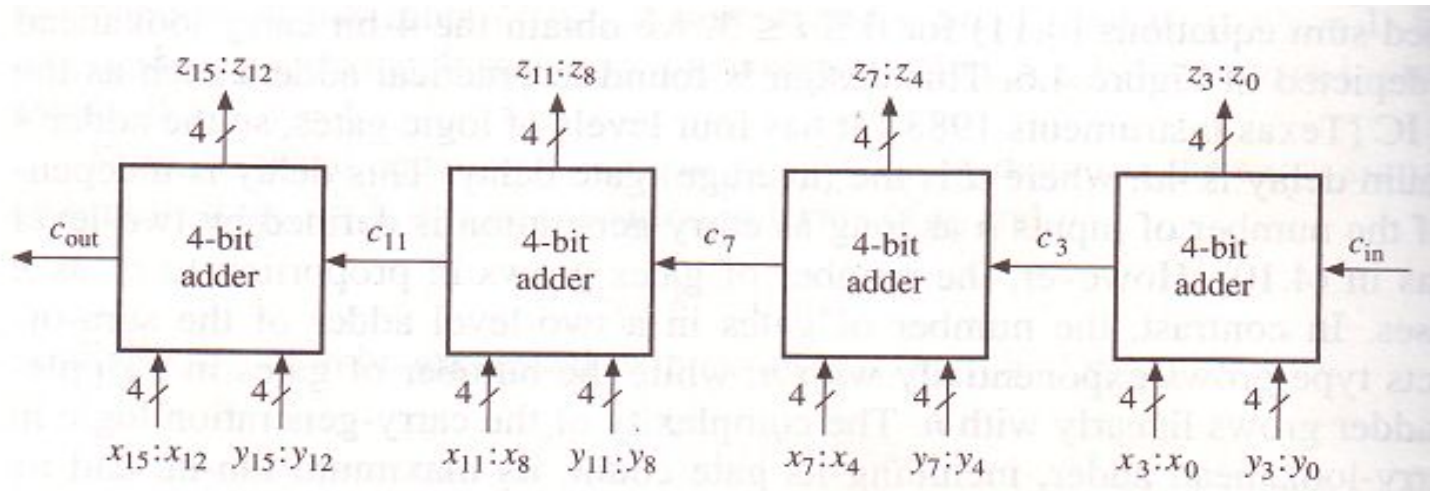- ✓ For sign-magnitude number, it is useful to construct a subtracter on the full (1-bit) subtracter function $z_i = x_i \text{ xor } y_i \text{ xor } b_{i-1}$



16 bit Adder

Overflow

- ✓ When the result of an arithmetic operation exceeds the standard word size n , overflow occurs.

- ✓ Example: let $n=8$ $X=11101011=\underline{235}_{10}$ and $Y=00101010=\underline{42}_{10}$
 $Z = X+Y = 11101011$

$$\begin{array}{r} + 00101010 \\ \hline 100010101 = \underline{21}_{10} \end{array} \quad C_7 = 1$$

$$C_7 Z = 100010101 = \underline{277}_{10} = 256_{10} + 21_{10}$$

- ✓ The result of an addition simply wraps around when the largest number 2^n-1 is exceeded.
- ✓ For n , the number range for unsigned number is 0 to 2^n-1

Overflow

✓ We can never have ~~overflow on adding~~ a negative and positive number.

✓ Example: let $n=8$ $X=11101011=-21_{10}$ and $Y=00101010=+42_{10}$

$$Z = X + Y = 00010101 = 21_{10} \quad C_7 = 1$$

So, $C_{n-1} = 1$ does not indicate overflow.

✓ Overflow in 2's complement addition can result from adding 1) two positive numbers or 2) two negative numbers.

✓ **Case 1:** Two numbers are positive.

Let $n=4$ $+7 = 0111$ $+3 = 0011$ so, $0111 + 0011 = \overset{\downarrow}{1}010$ so, $c_{n-2} = 1$

✓ $C_{n-2} = 1$ indicates that the magnitude of the sum exceeds the $n-1$ bits allocated to it.

Overflow

- ✓ **Case 2:** Two numbers are negative.

Let $n=4$ $-7 = 1001$ $-3 = 1101$ so, $1001+1101 = \overset{\downarrow}{1}\overset{\downarrow}{0}110$ so, $c_{n-2} = 0$

- ✓ $C_{n-2}=0$ indicates the overflow.


- ✓ For n the number for 2's complement number is $+(2^{n-1}-1)$ to -2^n .
- 

Overflow

- ✓ $Z_{n-1}Z_{n-2}\dots Z_0 := X_{n-1}X_{n-2}\dots X_0 + Y_{n-1}Y_{n-2}\dots Y_0$
- ✓ $v = X_{n-1}Y_{n-1}\overline{C_{n-2}} + \overline{X_{n-1}}\overline{Y_{n-1}}C_{n-2}$
- ✓ $v = C_{n-1} \text{ xor } C_{n-2}$

X_{n-1}	Y_{n-1}	C_{n-2}	Z_{n-1}	v
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

Ripple Carry Adder

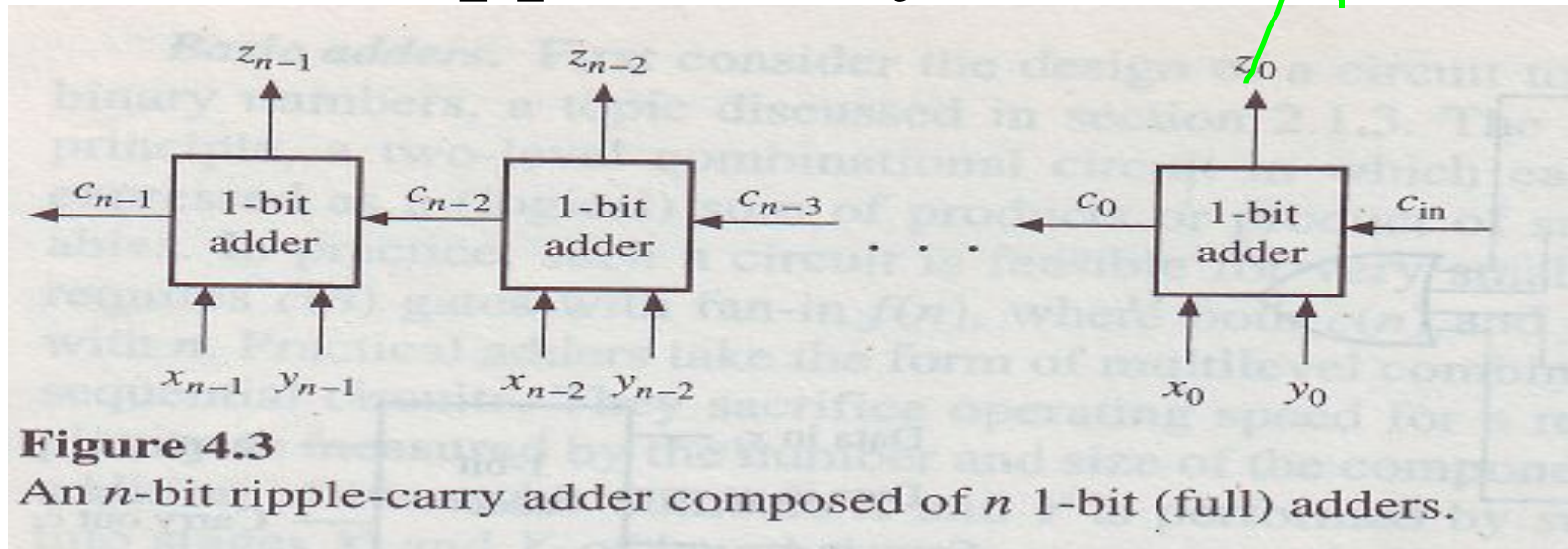


- ✓ the carry signal propagate through the adder from right to left
- ✓ The maximum signal propagation delay is nd , where d is the delay of a full-adder stage.

High Speed Adder

- ✓ Reduce the time required to form carry signals.
- ✓ **Approach:** To compute the input carry needed by stage i directly from carrylike signals obtained from all the preceding stages $i-1, i-2, \dots, 0$.
- ✓ Adders that use this principle are called carry-lookahead adders.

Carry Lookahead Adder

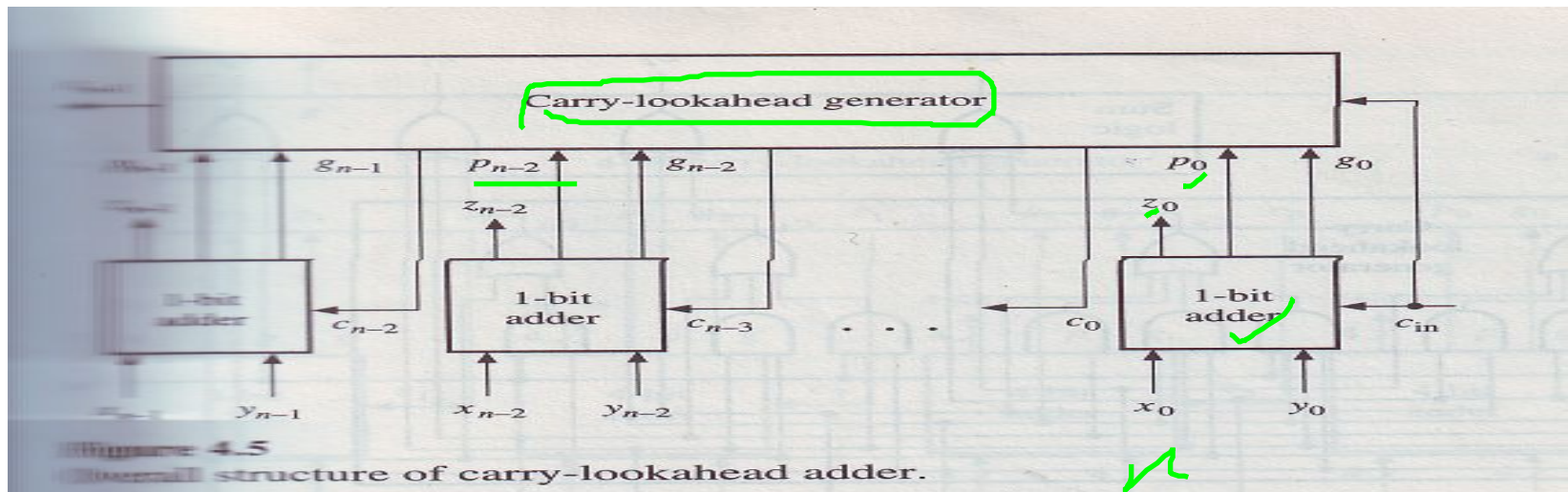

- ✓ generate signal $g_i = x_i y_i$ and propagate signal $p_i = x_i + y_i$
- ✓ $c_i = x_i y_i + x_i c_{i-1} + y_i c_{i-1}$ is the carry to be sent to the stage $i+1$.
- ✓ $c_i = g_i + p_i c_{i-1}$
- ✓ $c_{i-1} = g_{i-1} + p_{i-1} c_{i-2}$
- ✓ $c_i = g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-2}$

4-bit Carry Lookahead Adder

✓ $c_0 = g_0 + p_0 c_{in}$


$$c_1 = g_1 + p_1 g_0 + p_1 p_0 c_{in}$$

$$c_2 = \underline{g_2} + \underline{p_2 g_1} + \underline{p_2 p_1 g_0} + \underline{p_2 p_1 p_0 c_{in}}$$

$$c_3 = \underline{g_3} + \underline{p_3 g_2} + p_3 \underline{p_2 g_1} + p_3 p_2 \underline{p_1 g_0} + \underline{p_3 p_2 p_1 p_0 c_{in}}$$

✓ $z_i = \underline{x_i \text{ xor } y_i \text{ xor } c_{i-1}}$ can be written as $z_i = \underline{p_i \text{ xor } g_i \text{ xor } c_{i-1}}$

4-bit Carry Lookahead Adder

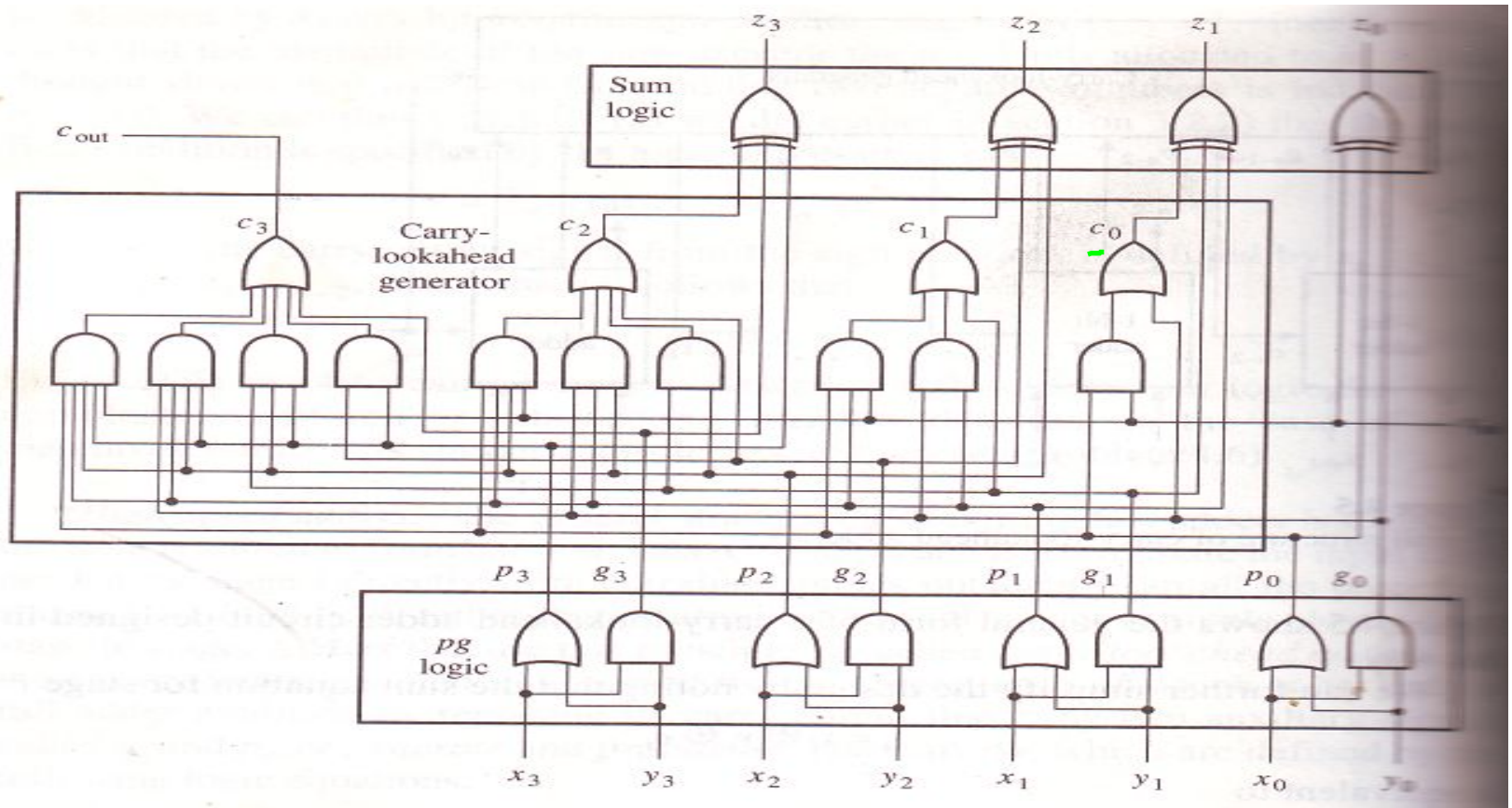

4-bit CarryLookahead Adder

- ✓ Maximum delay is $4d$, where d is the average gate delay. It is independent of number of input n .
- ✓ The complexity of the carry generation logic in the carry lookahead adder, including its gate count, its maximum fan-in, and its maximum fan-out, increase steadily with n .
- ✓ It limits n to 4.

Adder Expansion

- ✓ If we replace n 1-bit adder stages in the n -bit ripple carry adder with n k -bit adders, we obtain an nk -bit adder.


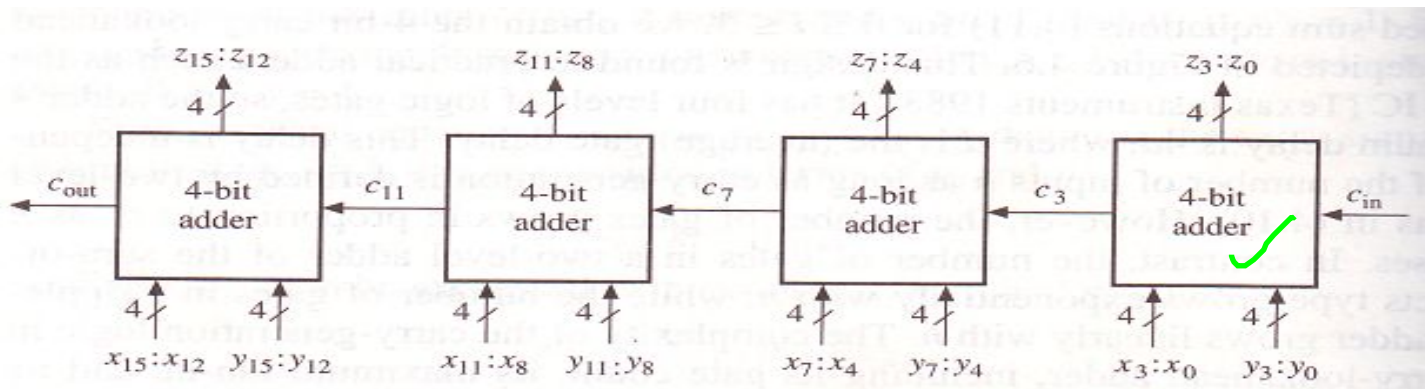


Figure: A 16-bit adder composed of 4-bit adders linked by ripple-carry propagation

Adder Expansion


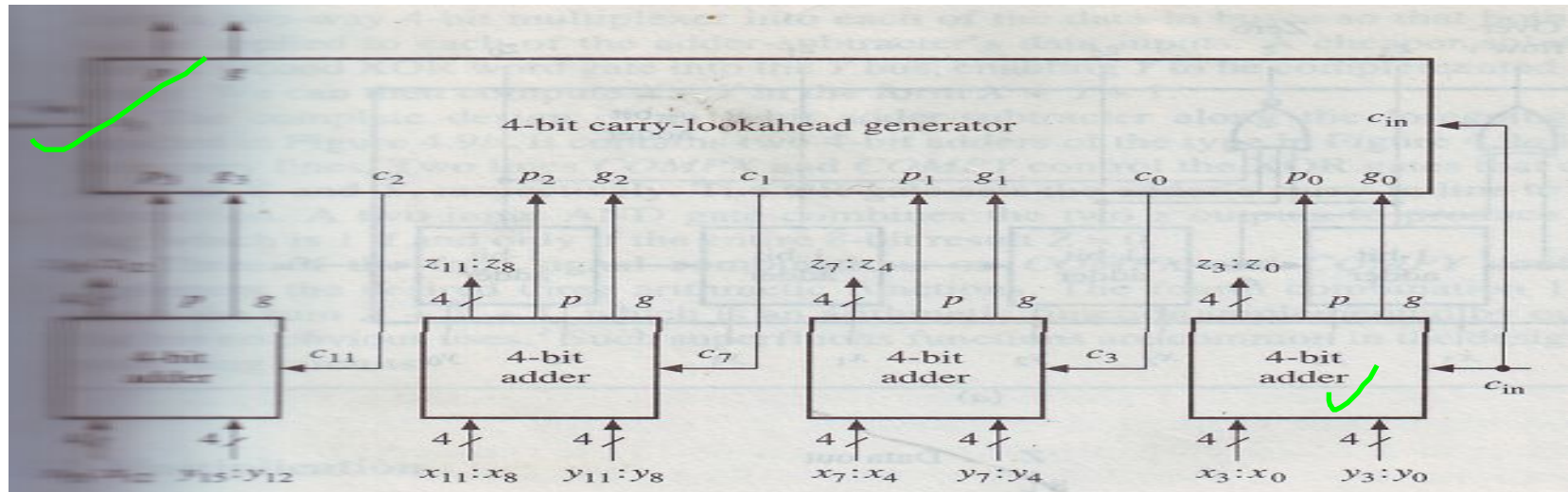


$$g = x_i y_i + x_{i-1} y_{i-1} (x_i + y_i) + x_{i-2} y_{i-2} (x_i + y_i) (x_{i-1} + y_{i-1})$$

$$+ x_{i-3} y_{i-3} (x_i + y_i) (x_{i-1} + y_{i-1}) (x_{i-2} + y_{i-2})$$

$$p = (x_i + y_i) (x_{i-1} + y_{i-1}) (x_{i-2} + y_{i-2}) (x_{i-3} + y_{i-3})$$

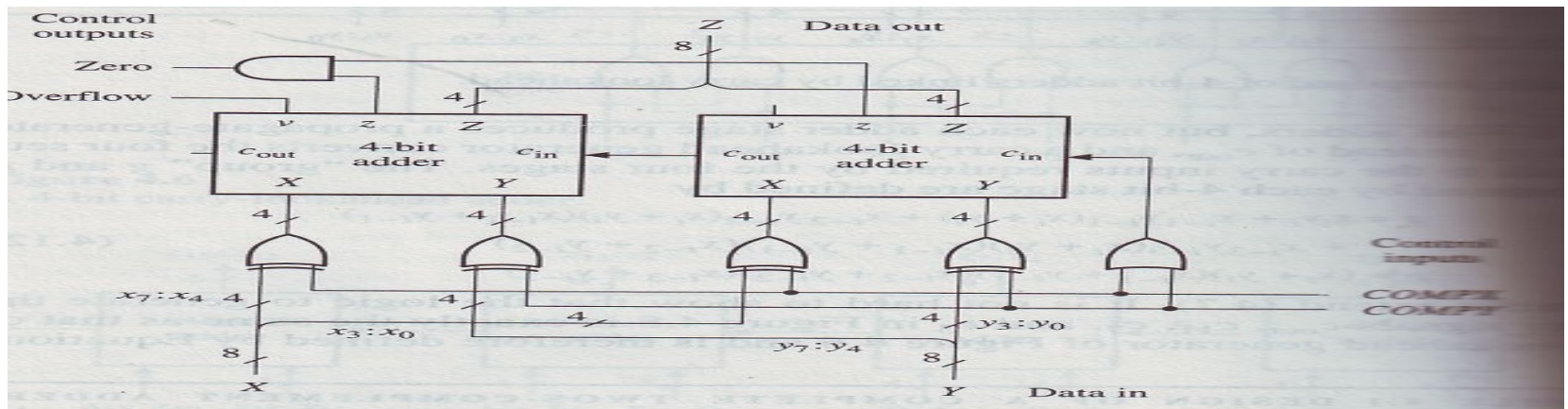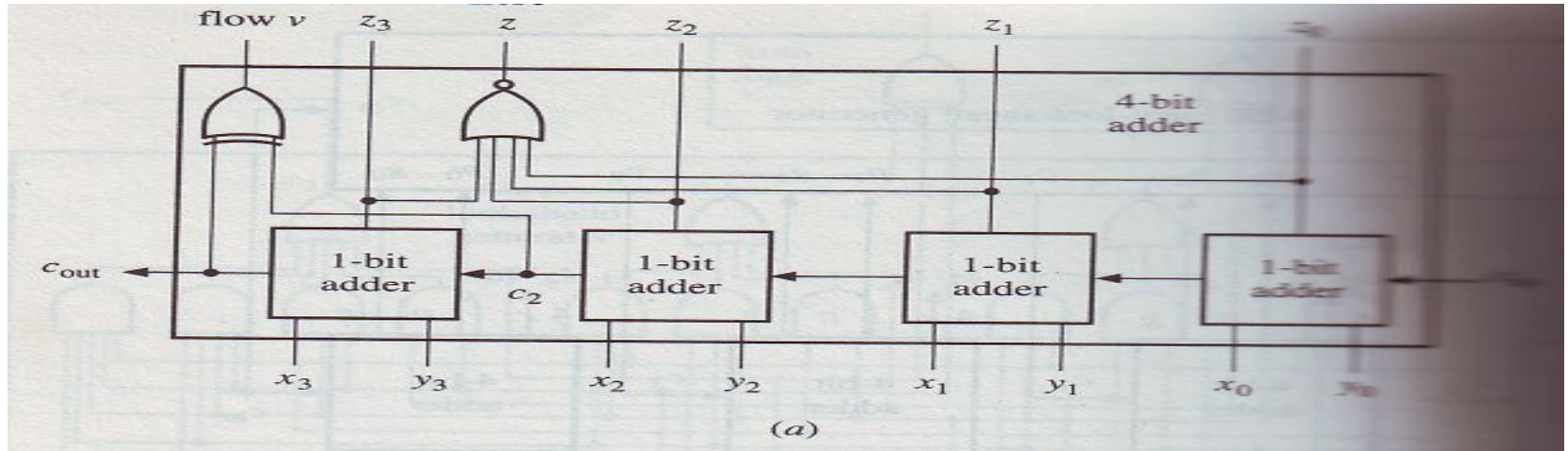Design of a Complete 2's Complement Adder-Subtractor



Chapter 4, Section 4.1 of John P. Hayes Book