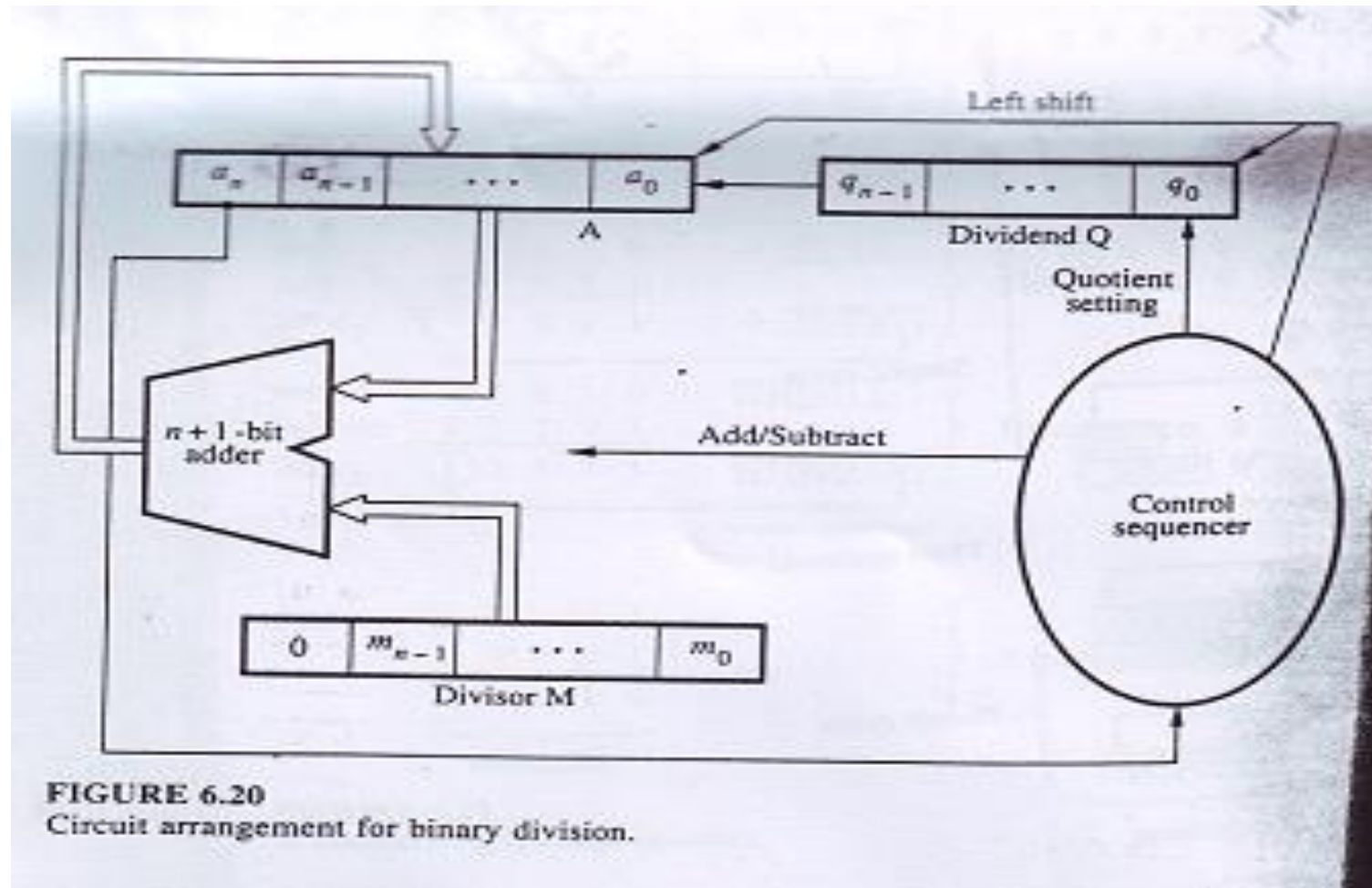


Datapath Design

Circuit Arrangement for Restoring Binary Division (Positive Numbers)




Restoring Division

1. Do the following n times:
 - (a) Shift A and Q left one binary position.
 - (b) Subtract M from A and place the result back in A .
 - (c) If the sign of A is 1, set q_0 to 0 and add M back to A ; otherwise, set q_0 to 1.

Note: Subtraction is performed by using 2's complement arithmetic.

Example

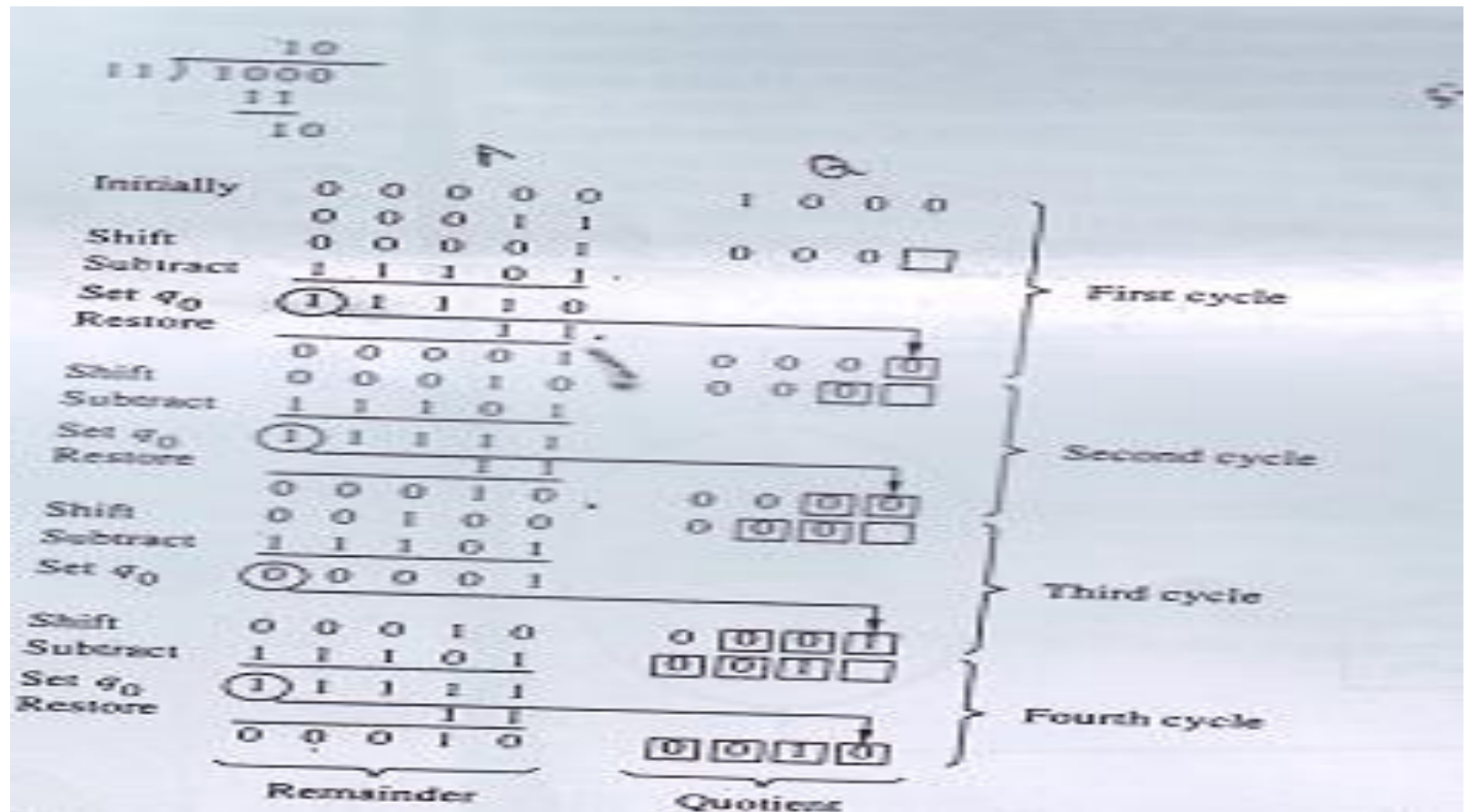

Non-restoring Division

- ✓ Restoring division algorithm can be improved by avoiding the need for restoring A after an unsuccessful subtraction.
- ✓ If A is positive, we shift left and subtract M . That is we perform $2A - M$.
- ✓ If A is negative, we restore it by performing $A + M$ and then we shift it left and subtract M . This is equivalent to $2A + M$.

Algorithm for non-restoring Division

Step 1:

Do the following n times:


if sign of A is 0, shift A and Q left one bit position and subtract M from A ; otherwise shift A and Q left and add M to A .

if the sign of A is 0, set q_0 to 1; otherwise set q_0 to 0.

Step 2:

if sign of A is 1, add M to A .

Example

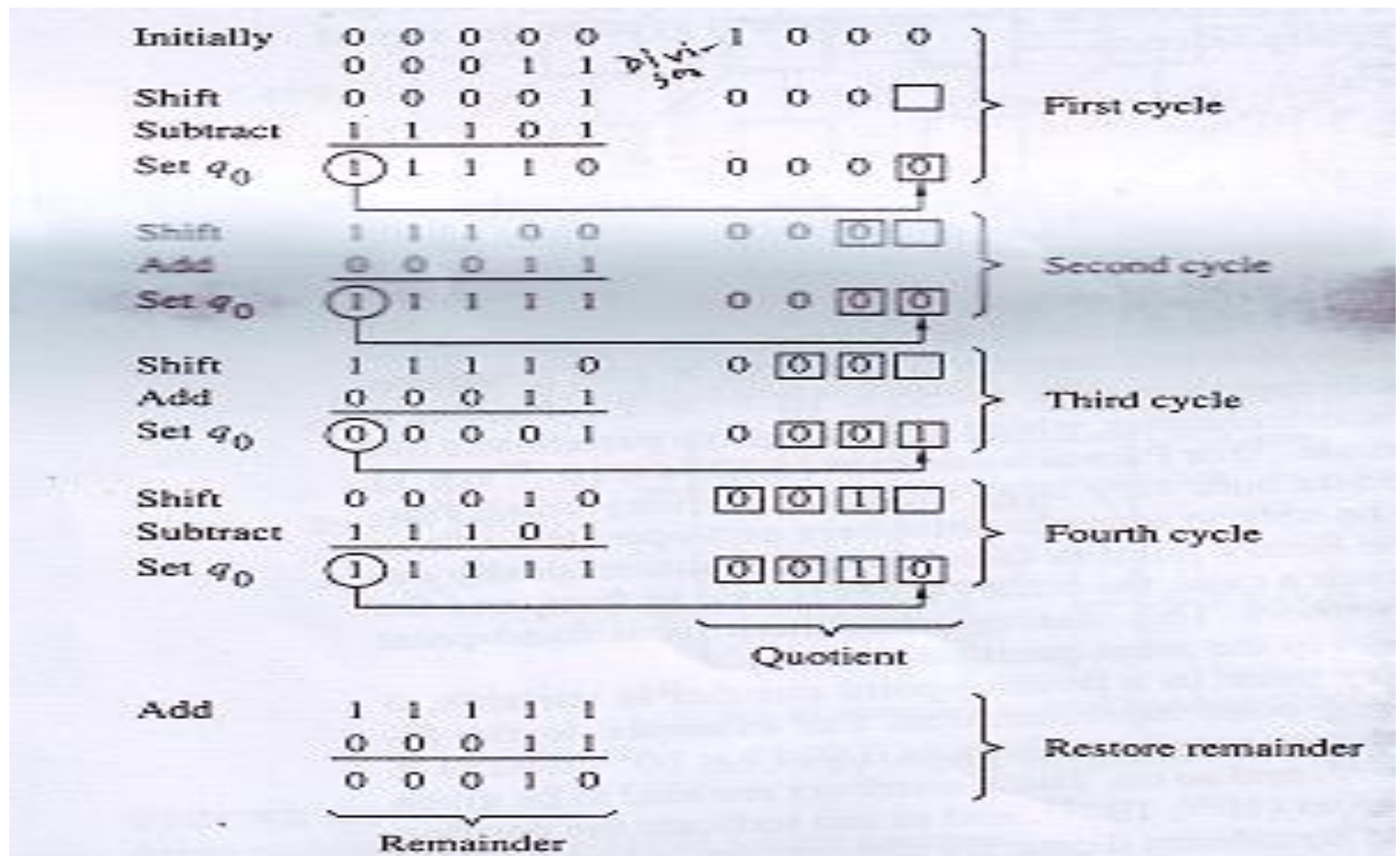


Signed Division

- Negate the quotient if the sign of the operands are opposite.
- Sign of the non-zero remainder should match the dividend.
- Example:
 - $+7 / +2 : Q= 3 \text{ and } R=1$
 - $-7 / +2 : Q= -3 \text{ and } R=-1$
 - $-7 / -2 : Q = 3 \text{ and } R = -1$
 - $+7 / -2: Q = -3 \text{ and } R = 1$


Carry Save Addition

- ✓ An n-bit carry save adder consists of n disjoint full adders.
It's input is three n-bit numbers to be added and the output consists of the n-sum bits forming a word S and the n carry bits forming a word C .
- ✓ Carry connections are shifted to the left correspond to normal carry propagation.
- ✓ To obtain the final result, S and C must be added by a conventional adder with carry propagation.

Carry Save Addition

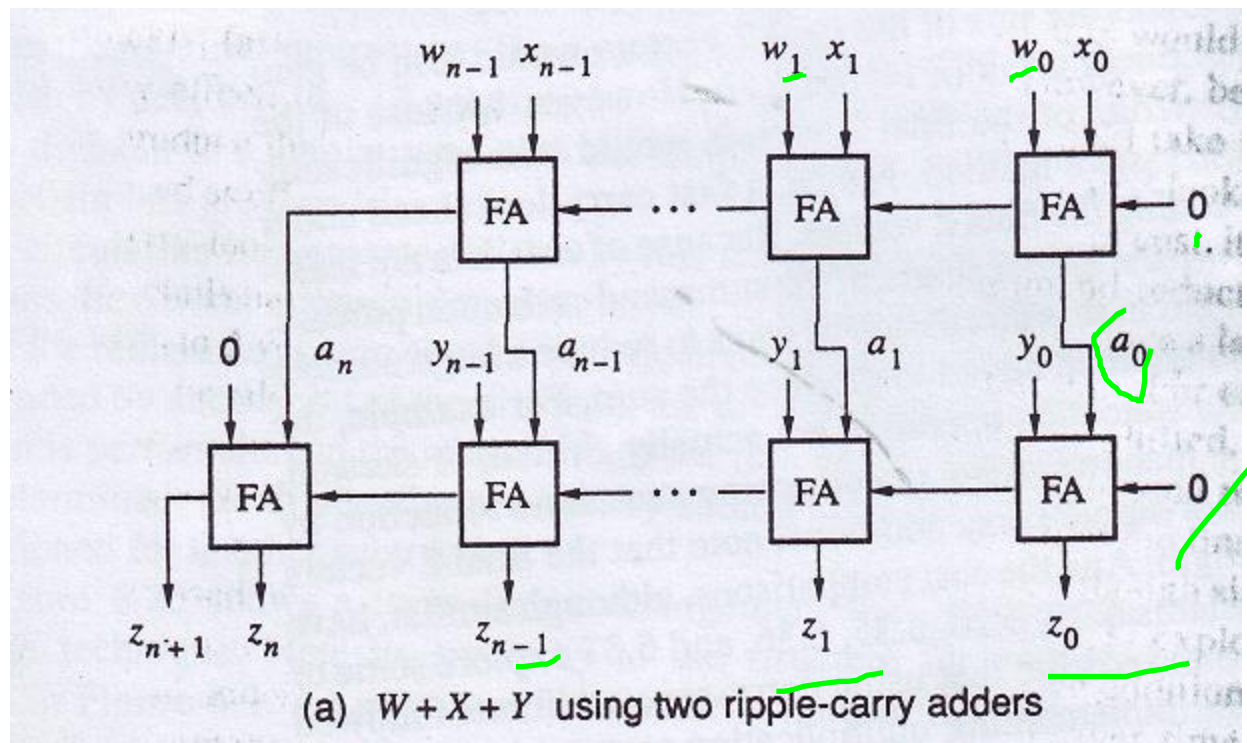

Carry Save Addition

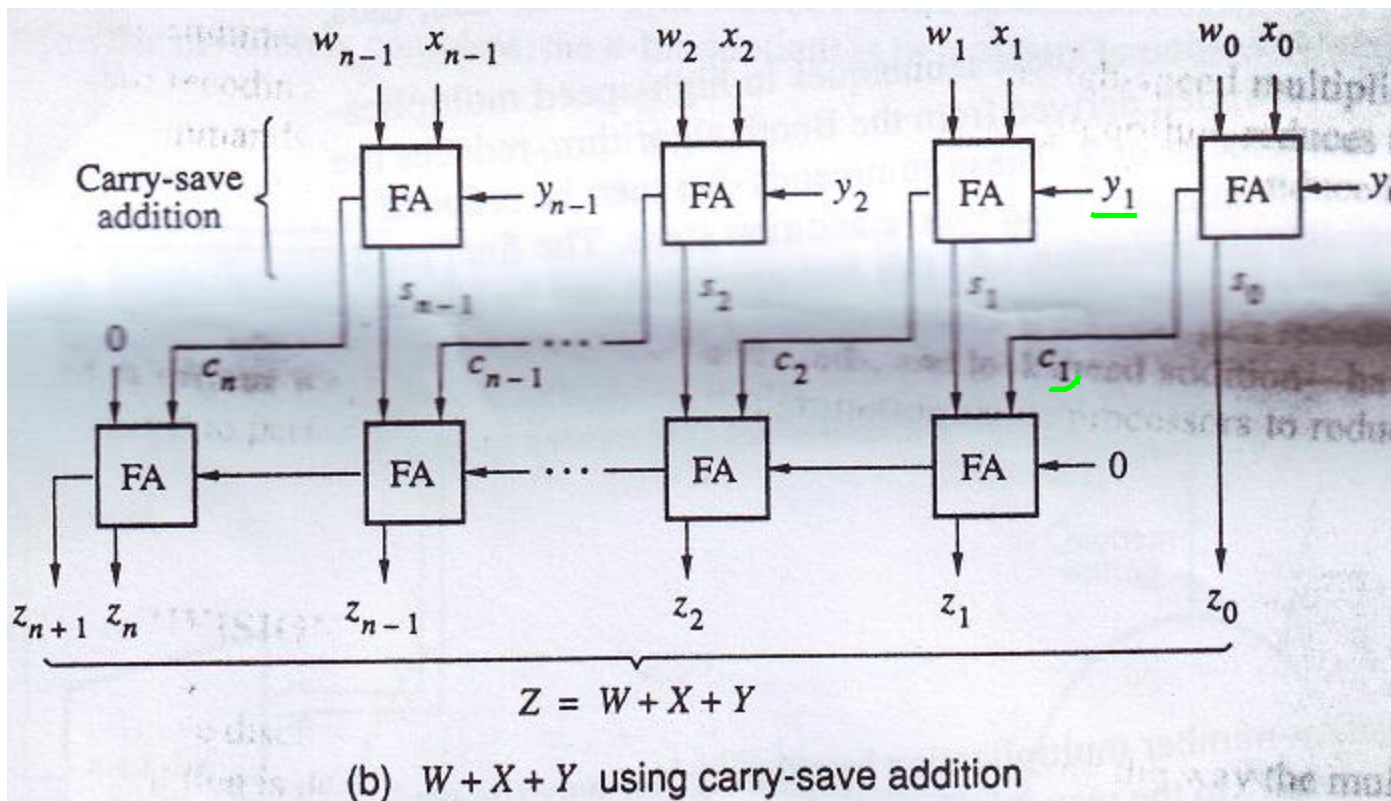

Carry Save Addition

$$\begin{array}{r}
 W \\
 + X \\
 \hline
 A \\
 + Y \\
 \hline
 Z
 \end{array}
 \Rightarrow
 \begin{array}{r}
 10101 \\
 + 11011 \\
 \hline
 110000 \\
 + 010100 \\
 \hline
 1000100
 \end{array}$$

Using the network in part (a)

Carry-save
addition

$$\begin{array}{r}
 W \\
 X \\
 + Y \\
 \hline
 S \\
 + C \\
 \hline
 Z
 \end{array}
 \Rightarrow
 \begin{array}{r}
 10101 \\
 11011 \\
 + 10100 \\
 \hline
 11010 \\
 + 10101 \\
 \hline
 1000100
 \end{array}$$

Using the network in part (b)

$$Z = W + X + Y$$

Carry Save Addition

Advantages:

- ✓ All bits of S and C vectors are produced in a short, fixed amount of time.
- ✓ Carry propagation takes place only in the second row.
- ✓ Since all bits of S and C are available in parallel, a carry-lookahead adder can be used effectively to add the S and C .